


1. We wish to recognize the sequence "110" using a Moore machine implementation.

(a) Determine the required number of states and their encoded values

4 states

$S_0$ : 0 bits of sequence detected	$S_0$ : 00
$S_1$ : 1 bit of sequence detected	$S_1$ : 01
$S_2$ : 2 bits " " " "	$S_2$ : 10
$S_3$ : 3 " " " "	$S_3$ : 11

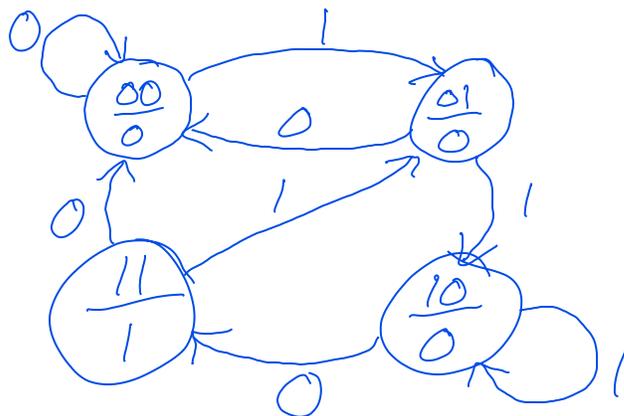(b) Draw the state transition diagram making sure you consider both input possibilities for each state



(c) Complete the state transition table

Present State		Input x	Next State		Output z
$q_1$	$q_0$		$q_1^+$	$q_0^+$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	0	1	1

(d) Derive the Boolean expressions for the next state variables

\*Fewer 1's than 0's  $\Rightarrow$  SOP

$$q_1^+ = \bar{q}_1 q_0 x + q_1 \bar{q}_0 \bar{x} + q_1 \bar{q}_0 x$$

simplifies to  $q_1 \bar{q}_0$

Not required, but...

$$q_1^+ = \bar{q}_1 q_0 x + q_1 \bar{q}_0$$


$$q_0^+ = \bar{q}_1 \bar{q}_0 x + q_1 \bar{q}_0 \bar{x} + q_1 q_0 x$$

$$Z = q_1 q_0 \bar{x} + q_1 q_0 x = q_1 q_0 (\bar{x} + x)$$

$$Z = q_1 q_0$$

(e) Sketch the hardware implementation

# of flip flops = # of state bits = 2

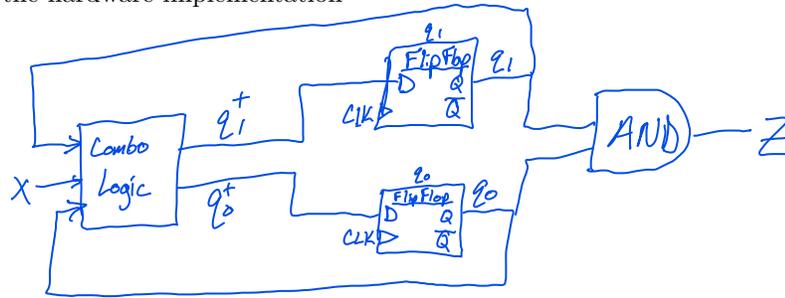

\*Since  $Z = q_1 q_0$ , I just used the AND gate instead of a generic "Combo Logic" box. Either way is correct.

2. We are confronted with a bit of a puzzle! The following digital padlock design has only been partially documented in terms of the state transition diagram and table.

- There are 4 states which must all be encoded with a 2-bit name
- Note, the state names are not at all derived from the lock combination!
- The input button push "B" can be 0 or 1.
- There are three numbers in the unlock code.


state	Encoded	#bits in Unlock sequence
S0	00	0
S1	10	1
S2	01	2
S3	11	3

(a) Complete the drawing of the state transition diagram (Note: there are 3 transitions missing, 2 states that need to be assigned, and 1 output value missing). Then fill in the remaining entries of the state transition table below.

$q_1$	$q_0$	B	$q_1^+$	$q_0^+$	Unlock
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	1

- Use the info in the transition diagram to complete the table and the info in the table to finish the diagram.

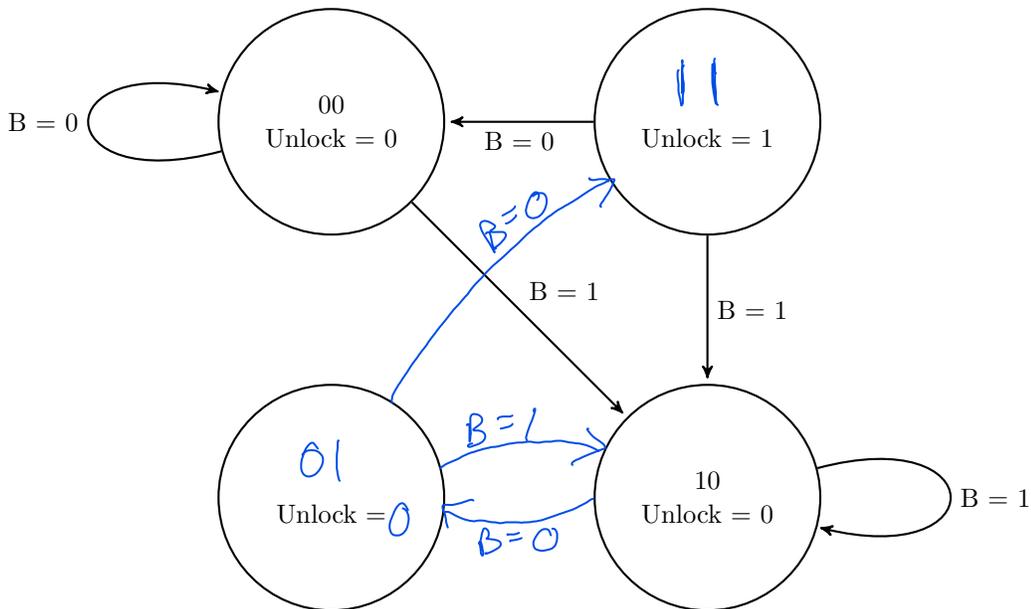- Moore machine since output Unlock inside state in diagram; easy to complete Unlock column in table!



(b) Specify the UNLOCK output from the table using a SOP Boolean expression

$$\text{Unlock} = q_1 q_0 \bar{B} + q_1 q_0 B = q_1 q_0 (\bar{B} + B) = q_1 q_0$$

(makes sense, since this a Moore machine and Unlock only equals 1 in state s3 (11).)

UNLOCK =

$$q_1 q_0$$

(c) Specify the  $q_1^+$  next state using a POS Boolean expression

$$q_1^+ = (q_1 + q_0 + B)(\bar{q}_1 + q_0 + B)(\bar{q}_1 + \bar{q}_0 + B)$$

3 0's in  $q_1^+$  column

$q_1^+$  POS =

$$(q_1 + q_0 + B)(\bar{q}_1 + q_0 + B)(\bar{q}_1 + \bar{q}_0 + B)$$

(d) What is the combination for the lock?

- Follow the input sequence needed to get to state s3 (11).

Combination =

$$100$$


Name:

Documentation:

1. A vending machine requires 15 cents for a tasty cup of coffee. It does not take pennies or quarters. It can provide a nickel in change. ← *Derived requirement: can only give change if also vending.*

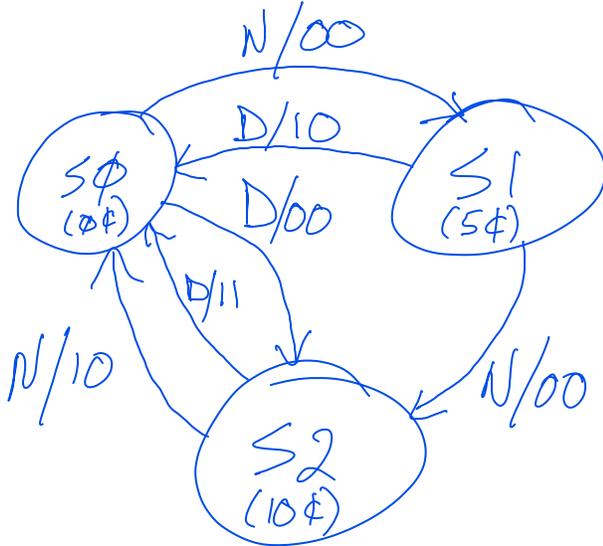(a) Draw the state transition diagram.

*Note: It should be a Mealy machine with 3 states, you should return to zero money when you vend*



Outputs	Meaning
00	No vend, no change
01	(unused)
10	vend, no change
11	vend, change

\* Mealy machine use INPUT/OUTPUT notation with each transition arrow

- (b) Encode the states and the inputs. The inputs should be N: nickel or D: dime. You can only input one coin at a time.

Inputs	Encoded	State	Encoded	Meaning
N	0	S0	00	no money
		S1	01	5¢
D	1	S2	10	10¢

- (c) Create the state transition table.

$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z_1$	$z_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	1	0
1	0	1	0	0	1	1
1	1	0	x	x	x	x
1	1	1	x	x	x	x

Use DON'T CARES for 4th unused state

(d) Write the next state and output logic expressions. \*Fewer 1's than 0's  $\Rightarrow$  SOP

$$q_1^+ = \bar{q}_1 \bar{q}_0 X + \bar{q}_1 q_0 \bar{X}$$

$$q_0^+ = \bar{q}_1 \bar{q}_0 \bar{X}$$

$$Z_1 = \bar{q}_1 q_0 X + \underbrace{q_1 \bar{q}_0 \bar{X} + q_1 \bar{q}_0 X}_{\text{simplifies}}$$

$$Z_1 = \bar{q}_1 q_0 X + q_1 \bar{q}_0$$

$$Z_2 = q_1 \bar{q}_0 X$$

(e) Implement the design in hardware. # Flip Flops = # of bits for states = 2

